

Stopwatch implementation

Hardware Acceleration with FPGA

Speaker: Felipe Tortato

- Presentation (10 min):
 - Solution Structuring
 - Simulation Results
 - Synthesis and Implementation
- Questions and discussion (10 min)

- Notation:

- '1' represents "active state" in the diagram
- Transition of states happens with rising edge clock (AND specified signal)
- If reset is active, current state will always be the starting one, independent on other inputs

 


Figure 2: State diagram of the stopwatch (as example)

- Debouncer: Finite state machine with 3 states
 - START: beginning of execution, when button reset is pressed
 - IDLE: waiting for button press. The counter of cycles is cleared
 - WAITING: cycle counter is incremented every cycle while key is still pressed until reaching the limit. If key is released, it comes back to idle state. If the limit was achieved, a pulse of 1 cycle is set at the output, otherwise, the output remains at '0'

 


Figure 3: State diagram of the debouncer

- TDM: Finite state machine with 5 states
 - RESET: beginning of execution, when button reset is pressed. Counter of cycles is cleared
 - TD1: cycles are incremented until the limit is reached (time slot duration), then changes to TD2. The output is for the display 1
 - TD2: cycles are incremented until the limit is reached, then changes to TD3. The output is for the display 2
 - TD3: cycles are incremented until the limit is reached, then changes to TD4. The output is for the display 3
 - TD4: cycles are incremented until the limit is reached, then changes to TD1. The output is for the display 4

 


Figure 4: State diagram of the TDM

- SW: Finite state machine with 4 states
 - START: beginning of execution, when button reset is pressed. Cycles, seconds, tens of seconds, minutes and tens of minutes are cleared
 - RUN: cycles are incremented until a second is reached and then tens of seconds, minutes and tens of minutes are calculated
 - PAUSE: cycles are not incremented, but the value remains the same as the last cycle at RUN state
 - CLEAR: cycles, seconds, tens of seconds, minutes and tens of minutes are cleared. Comes back automatically to RUN state after one cycle


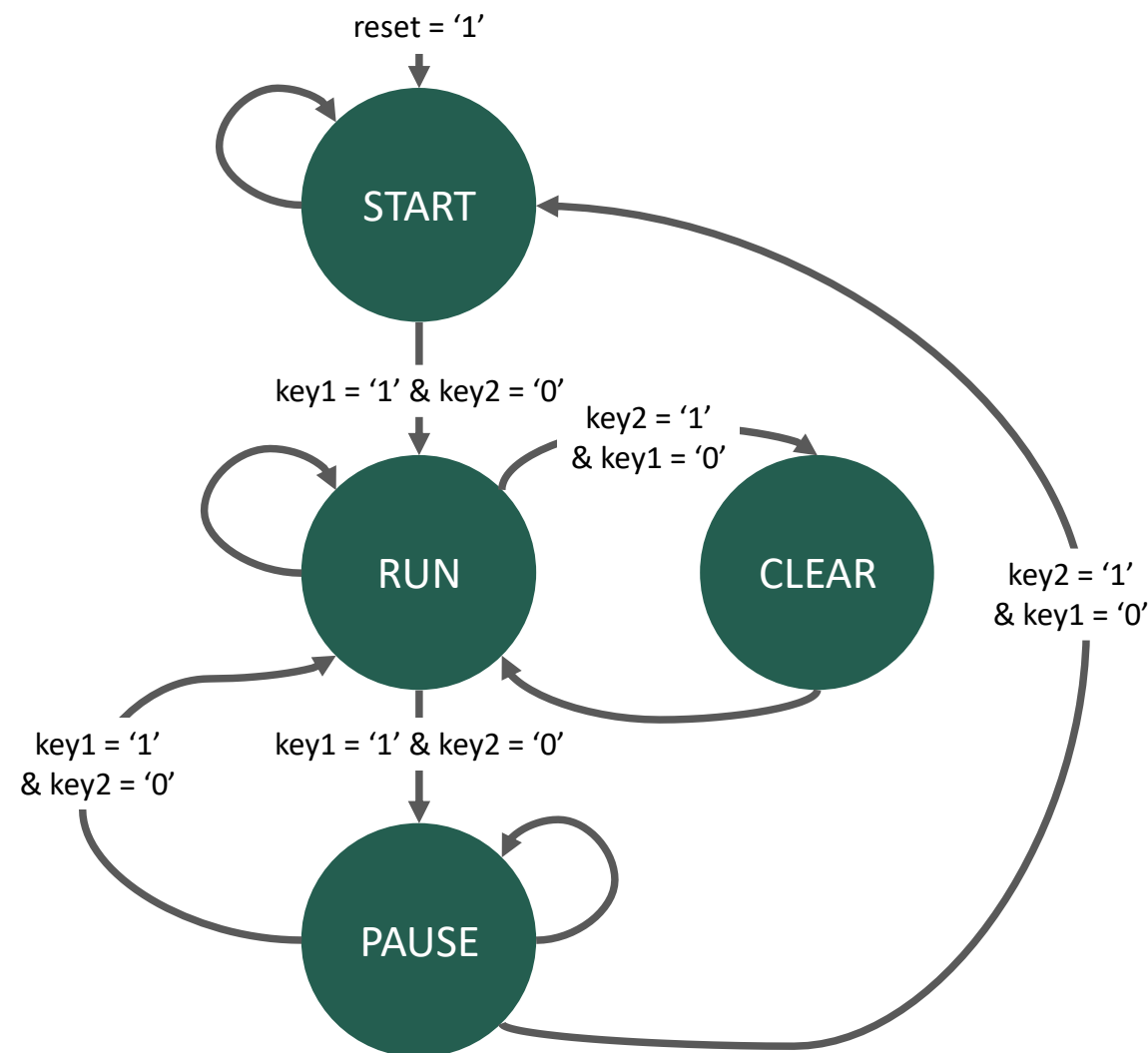
 


Figure 5: State diagram of the stopwatch


- Structuring of testbench simulations
 - 7-segment display decoder (testbench given):
 - input of 4 bits is changed with numbers from 0x0 to 0xF -> the output is observed
 - Button debounce:
 - input is set to active for a smaller number of cycles than required -> the output is observed
 - input is set to active for the exact number of cycles required -> the output is observed
 - Input is set to active for a bigger number of cycles than required -> the output is observed
 - Time division multiplexer:
 - input is fixed with the numbers -> change in the output with time is observed
 - one of the input changes -> change in this time slot is observed
 - SW (Stopwatch controller + debounce + decoder):
 - variation of states using key1 and key2 -> displays are observed for a long number of cycles
- Use of generic was important to be able to easily change configuration of time for the test benches

- 7-segment display Decoder ✓

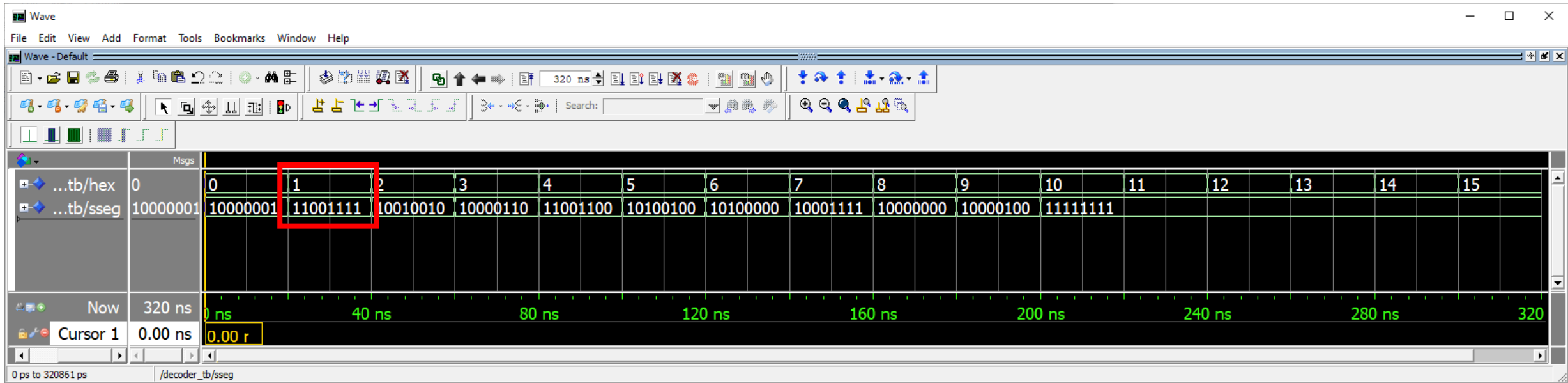

dp a b c d e f g
(7) ... (0)


• Button Debounce ✓

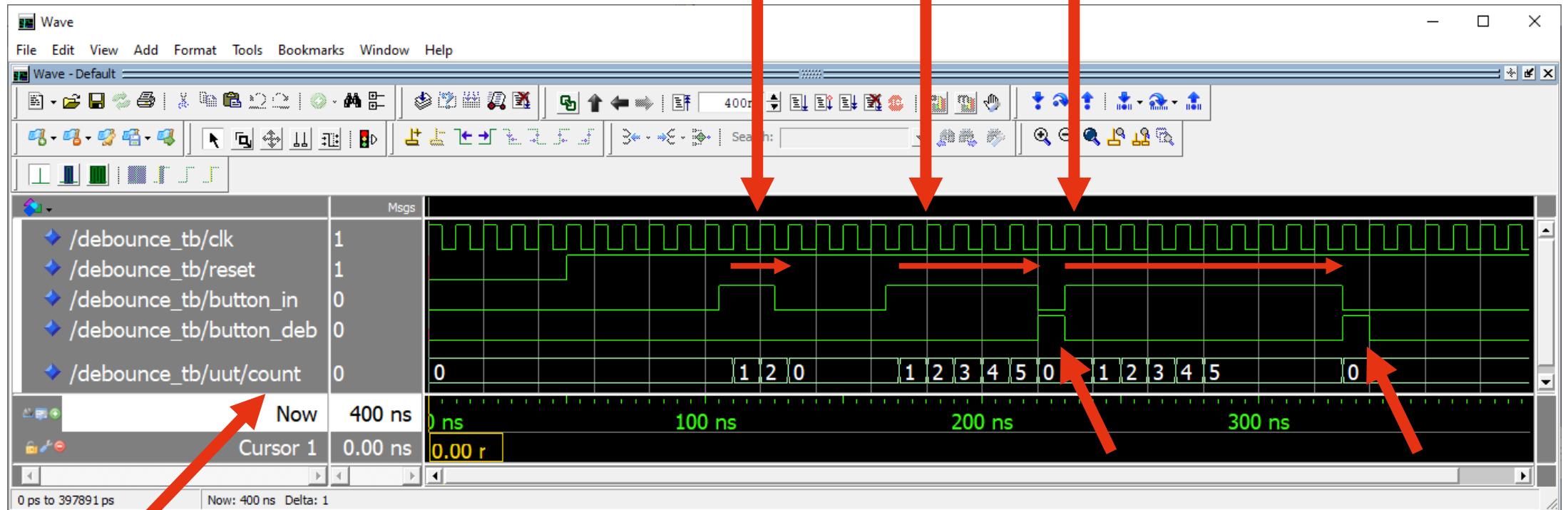

Internal signal
(debug only)

Button needs to be detected in active state for at least N (sim: 5) rising clock cycles, and need to stay one cycle at inactive state to produce the output

• Time Division Multiplexer ✓

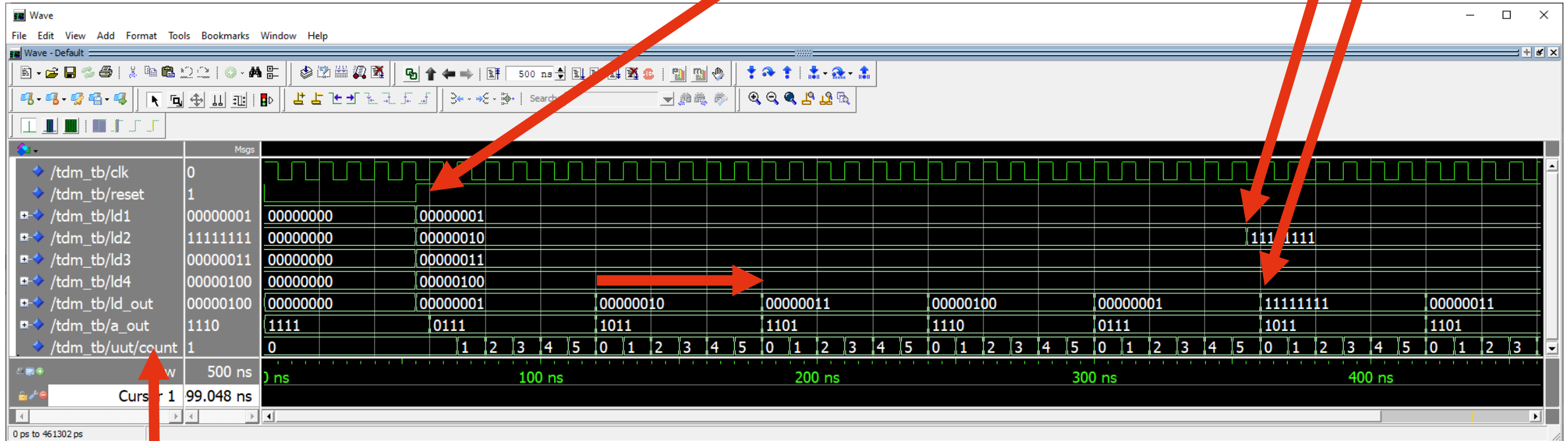

- Stopwatch: key1 press, state change (start->run), counter increase

Key1 is pressed

Debounce of key1
sends a pulse


Change of current
state 1 cycle after

Change of next state
with key1 press

Increment in
counter of cycles

Key1 is released

 Increment in
counter of
seconds and
output update



Summary per component:

	Decoder	Debounce	TDM	Stopwatch
States	-	3	5	4
Transitions	-	7	9	11
D-Type FFs	-	2	1	42
Adder/Subtractor	-	-	-	5
Comparators	-	-	1	4
Counters	-	1	1	-
ROMs	1	-	-	-
State Encoding	-	gray	one hot	gray

Macro statistics:

Counters of
controller
interpreted as
registers



	Total	Used at
Registers	7	
1-bit	2	Stopwatch controller and TDM
4-bit	4	Stopwatch controller
25-bit	1	Stopwatch controller
Adders/Subtractors	5	
4-bit adder	4	Stopwatch controller
25-bit adder	1	Stopwatch controller
ROMs	4	
16x8-bit	4	Decoder
Counters	3	
5-bit up	2	Debounce
17-bit up	1	TDM
Comparators	5	
4-bit less	4	Stopwatch controller
17-bit less	1	TDM

Device utilization (map report):

- Number of Slices: 132/3584 (3%)
- Number of Slice Flip Flops: 100/7168 (1%)
- Number of 4 input LUTs: 233/7168 (3%) – logic: 176; route-thru: 57
- Number of IOs: 16
- Number of bonded IOBs: 16/97 (16%)
- Number of GCLKs: 1/8

Timing report:

- Minimum period: 7,751 ns
 - controller/current_state_FSM_FFd2 to controller/counter_tens_minutes_1
 - controller/current_state_FSM_FFd2 to controller/counter_tens_minutes_2
- Maximum allowed clock frequency: 129,016 MHz
- Worst case slack:
 - Setup: 42,249 ns
 - Hold: 0,757 ns
 - time_multiplexer/current_state_FSM_FFd4 to time_multiplexer/current_state_FSM_FFd2

- Solution worked
 - Adjustments in the debounce time and in the order of the displays were required before having a full working version
- Better structuring of the solution before start of development
 - Need of TDM only noticed after almost everything was ready
 - Optimization in state machines could lead to a smaller number of bits required for representation
 - Lack of experience led to adaptations to get it working
 - TDM before the decoder could have used less hardware
- Automatization of the test procedure
 - Checking outputs in the test bench, for validation without need of visual check

Thank you!

Hardware Acceleration with FPGA

Speaker: Felipe de Souza Tortato